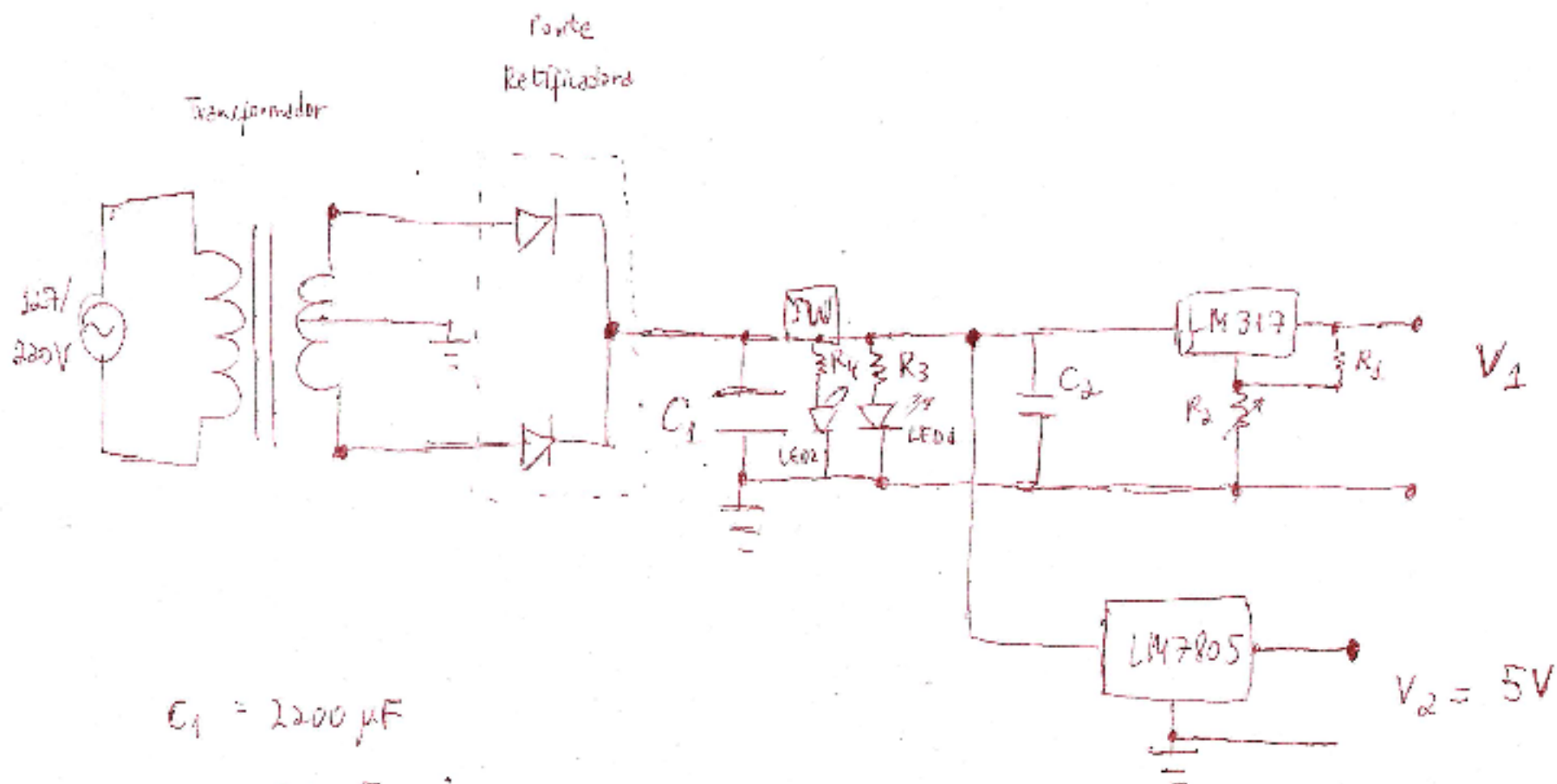




$$C_1 = 2200 \mu F$$

$$C_2 = 0,1 \mu F$$

$$R_1 = 220 \Omega$$

$$R_2 = 5k\Omega (\text{Pot})$$

$$R_3 = 500 \sim 1k\Omega$$

SW

SW (Chave Liga desliga)

LED1 (verde)

LED2 (vermelho)